

For regenerative braking of dc motor, which of the following choppers are suitable 1 point

- ☐ Type A
- ☐ Type B
- ☒ Type C
- ☐ Both Type A and Type B

Clear selection

In a two-quadrant chopper operating in 1st and 4th quadrants, the condition for zero output voltage is 1 point

- ☒ Times when output current is zero.
- ☐ During regenerative braking
- ☐ Output Power is same as input power
- ☐ Equal turn On and turn OFF times

Clear selection

A triangular signal with a peak value of 25 units is to be compared with a DC signal of K units such that gate signal is to be issued as long as dc signal is less than 25 units. If the duty cycle is to be maintained at 0.75, then the value of K is? 1 point

- ☐ 20
- ☐ 25
- ☐ 18.75
- ☐ 15.25



A type A chopper is feeding an RLE load with $V_s = 100V$, $E = 30V$, $R = 10$ Ohms. L is sufficiently large to make current continuous. At this condition, what is the value of duty cycle of the chopper to make thyristor current to be ripple free? 3 points

- ☐ 0.3
- ☐ 0.15
- ☐ 0.1
- ☐ 0.5

In a Type C chopper, the action of free wheeling diode is revealed during 1 point

- ☒ 1st quadrant operation
- ☐ 2nd quadrant operation
- ☐ Both 1st and 2nd quadrant operations
- ☐ None

Clear selection



A resistor of 10 Ohms, is connected to an AC supply of 230V, 50 Hz through a controlled switch. If the switch is controlled through a 10 kHz constant frequency based chopper control with 20% Turn-off duration, then the duty cycle is

1 point

- ☐ 0.2
- ☐ 1
- ☐ 0.01
- ☒ 0.8
- ☐ Other:

Clear selection

In an ideal step-up chopper operation, which one of the following statement is true

1 point

- ☒ source current is greater than load current
- ☐ source voltage is greater than load voltage
- ☐ Input power must be greater than output power
- ☐ none of the above

Clear selection

In a loss-free boost regulator feeding $R = 10$ ohms with $V_s = 100V$, the duty ratio is set at 40%. The average inductor current is

1 point

- ☐ 0.1 A
- ☐ 10 A
- ☐ 27.77 A
- ☐ 20.23 A



A copy of your responses will be emailed to f20190614@hyderabad.bits-pilani.ac.in.

Submit

Clear form

Never submit passwords through Google Forms.

This form was created inside of BITS Pilani University. [Report Abuse](#)

Google Forms

